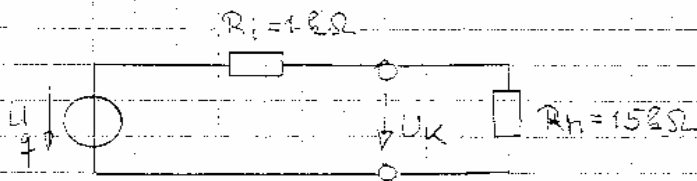


4.1 Spannungsmessung



$$a) \underline{U_k = U_g \frac{R_H}{R_i + R_H} = U_g \frac{1}{1 + R_i/R_H}}$$

$$\underline{U_g = U_k (1 + R_i/R_H)}$$

$$\underline{U_g = 10,67V}$$

$$b) F_{rel} = \frac{U_{k,ist}}{U_{k,son}} - 1 = \frac{U_k(R_H)}{U_k(R_H \rightarrow \infty)} - 1$$

$$F_{rel} = \frac{1}{1 + R_i/R_H} - 1 \approx - \frac{R_i/R_H}{1} \Rightarrow R_H \geq \frac{R_i}{|F_{rel}|} = \underline{1000 \Omega}$$

4.2 Strommessung mit Kompensationschaltung

$$a) P = U \cdot I \Rightarrow \underline{I = 0} \quad | \quad R_H = 0 \Omega$$

b) Nullinstrument wird Stromlos d.h.  $I_G = 0 \Rightarrow \Delta U = U_G = 0$

$$c) \begin{cases} I_x + I_N - I_H = 0 \\ I_x R_V = (I_H - I_x) R_N \end{cases}$$

$\hookrightarrow$  auf  $U_G = 0$ :  $U_{R_V} = U_{R_N}$

$$\underline{I_x = I_H \frac{R_N}{R_N + R_V}}$$

$$d) \Delta I_x = \frac{\partial I_x}{\partial R_N} \Delta R_N + \frac{\partial I_x}{\partial R_V} \Delta R_V + \frac{\partial I_x}{\partial I_H} \Delta I_H$$

$$= \frac{R_V}{(R_N + R_V)^2} \cdot 0,01\% R_N + \frac{-R_N}{(R_N + R_V)^2} \cdot 0,01\% R_V + \frac{R_N}{R_N + R_V} \cdot 0,2\% I_H$$

4.4 Messbereichserweiterung

a) Klemme A: 1 mA; 100 mV      Klemme B: 1 V

$$b) \text{Sperrteiler} \quad R_V = \frac{100 \text{ mV} - I_0 R_H}{I_0 R_H} = \underline{3 R_H = 150 \Omega}$$

$$\text{Stromteiler} \quad I_0 = I_{R_1} = 0,5 \text{ mA} \Rightarrow R_1 = R_V + R_H = \underline{200 \Omega}$$

$$\text{Spannteiler} \quad U_{R_2} = 0,3 \text{ V} \Rightarrow R_2 = 30 \cdot 100 \Omega = \underline{3 \pm 30 \Omega}$$

H.5

$$a) U_{ri} \equiv \bar{u} = \frac{1}{T} \int_0^T u dt = 0V, \quad U_G = |\bar{u}| = \frac{1}{T} \int_0^T |u| dt = \frac{2}{T} \hat{U} = 0,637 \hat{u}$$

$$U_{eff} = \sqrt{\frac{1}{T} \int_0^T u^2 dt} = \frac{\hat{u}}{\sqrt{2}} = 0,707 \hat{u}$$

230V-Netz:  $U_{eff} = 230V, \quad \hat{u} = \sqrt{2} \cdot 230V = 325,3V, \quad U_G = 207,2V$

b)  $\underline{k_2} = U_{eff} / U_G = 1,11$

4.6  $\square$  mit idealen Gleichrichter zeigt primär Gleichrichterlast an

• Aussage  $U_D = k_2 |\bar{u}| = 1,11 |\bar{u}|$

a) Formfaktor  $k_2 = \frac{U_{eff}}{|\bar{u}|}$  zur beliebigen Kurvenformeln

$$\Rightarrow U_D = \frac{1,11}{k_2} U_{eff}$$

b)  $\textcircled{1}$   $U_{eff}^2 = \frac{4}{T} \int_0^{T/4} \left( \frac{U \cdot t}{T/4} \right)^2 dt = \frac{U^2}{3} \Rightarrow U_{eff} = \frac{U}{\sqrt{3}} = 0,577 U$

$|\bar{u}| = \frac{4}{T} \int_0^{T/4} \frac{U t}{T/4} dt = \frac{U}{2} \Rightarrow U_D = \frac{1,11}{2} U = 0,555 U$

~~$\textcircled{2}$  wie  $\textcircled{1}$~~

$\textcircled{3}$   $U_{eff} = 0, \quad |\bar{u}| = 0 \Rightarrow U_D = 1,11 U$

$\textcircled{4}$  wie  $\textcircled{3}$  falls symmetrisch zur t/T-Achse  
i. allg.  $U_{eff}, |\bar{u}|$  von t/T abhängig.